

INTERNATIONAL INSTITUTE OF INFORMATION TECHNOLOGY
BANGALORE

VLSI PROJECT ELECTIVE

**VARIABLE PRECISION APPROXIMATE
FLOATING POINT MULTIPLIER**

B Sathiya Naraayanan
(IMT2020534)

November 22, 2023



INTRODUCTION

The Variable-precision approximate floating-point multiplier is proposed for energy efficient deep learning computation. The proposed architecture supports approximate multiplication with BFloat16 format. The approximation is done in form of truncation.

ARCHITECTURE

The inputs are divided into sign bits, exponent and mantissa bits separately. There are three block rams used, one for each inputs and one for the output. Sign and exponent module is used for getting the sign and exponent of the multiplied result. The calculated exponent is used for creating mask which is used to decide the number of bits to be truncated. This is done using precision control module. The mantissas are given as input to booth multiplier after appending '01' bits. The '1' bit is the implied bit that comes before the decimal point. The booth multiplication algorithm uses input in signed format, so '0' bit is added. All the outputs are processed and normalized for final output in the normalization module.

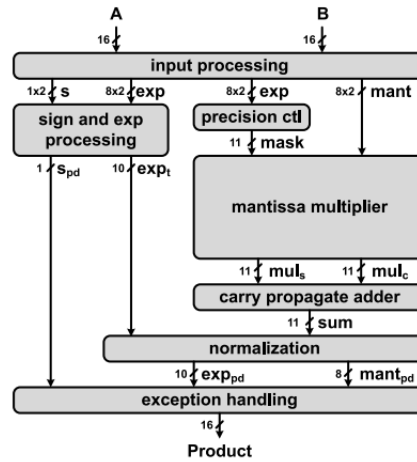


Figure 1: Multiplier Architecture

IMPLEMENTATION

The proposed architecture was implemented in verilog and implemented on Xilinx basys-3 fpga board using vivado. The multiplier was implemented without masking and precision control unit for comparing the results.

The verilog implementation of the multiplier with masking is as follows.

```

////////////////////////////////////
module float_mul(input [0:15] num1,input [0:15] num2,output [0:15] out);

    wire s1,s2;
    wire [0:7] ex1,ex2;
    wire [0:8] m1,m2;

    wire s;
    wire [0:9] exp;
    wire [0:10] mant;
    wire [0:10] mask;
    wire [0:9] exponent;
    wire [0:6] mantissa;

    assign s1=num1[0];
    assign s2=num2[0];
    assign ex1=num1[1:8];
    assign ex2=num2[1:8];
    assign m1={2'b01,num1[9:15]};
    assign m2={2'b01,num2[9:15]};

    sign_exp se(s1,s2,ex1,ex2,s,exp);
    prec_ctrl pc(exp,mask);
    booth_mul bm(m1,m2,mask,mant);
    normal nz(mant,exp,exponent,mantissa);

    assign out={s,exponent[2:9],mantissa};
endmodule

module sign_exp(input s1,input s2,input [0:7] ex1,input [0:7] ex2,output s,output [0:9] exp);
    assign s=s1^s2;
    assign exp={2'b0,ex1}+{2'b0,ex2}-10'd254;
endmodule

module normal(input [0:10] mant,input [0:9] exp,output [0:9] exponent,output [0:6] mantissa);
    assign mantissa=mant[2:8];
    assign exponent=exp+1'b1+10'd127;
endmodule

module prec_ctrl(input [0:9] exp,output reg [0:10] mask);
    wire [0:3] rg;
    assign rg=exp[2:5];
    always@(*) begin
        case(rg)

```

```

4'b0000:mask=11'b1111111111;
4'b0001:mask=11'b1111111110;
4'b0010:mask=11'b1111111100;
4'b0011:mask=11'b1111111000;
4'b0100:mask=11'b1111110000;
4'b0101:mask=11'b1111100000;
4'b0110:mask=11'b1111000000;
4'b0111:mask=11'b1110000000;
4'b1000:mask=11'b1110000000;
4'b1001:mask=11'b1111000000;
4'b1010:mask=11'b1111100000;
4'b1011:mask=11'b1111110000;
4'b1100:mask=11'b1111111000;
4'b1101:mask=11'b1111111100;
4'b1110:mask=11'b1111111110;
4'b1111:mask=11'b1111111111;
default:mask=11'b1111111111;
endcase
end
endmodule

```

```

module booth_mul(input wire [8:0] A,
                 input wire [8:0] B,
                 input [10:0] mask,
                 output wire [10:0] P);
    reg [2:0] bits[4:0];
    reg [9:0] pp[4:0];

    //wire [10:0] p1,p2,p3,p4;
    wire [8:0] A_;//minus A
    wire [15:0] pp1;
    wire [15:0] pp2;
    wire [15:0] pp3;
    wire [15:0] pp4;
    wire [15:0] pp5;
    integer m1;
    assign A_ = ~A + 1;

    always@(A or B or A_) begin

        bits[0] = {B[1], B[0], 1'b0};
        bits[4] = 3'b001;

        for(m1=1; m1<4; m1=m1+1)
            bits[m1] = {B[2*m1+1], B[2*m1], B[2*m1-1]};

        for(m1=0; m1<5; m1=m1+1) begin

```

```

        case(bits[m1])

            3'b001:pp[m1]={1'b0,A};
            3'b010:pp[m1]={1'b0,A};
            3'b011:pp[m1]={A,1'b0};
            3'b100:pp[m1]={A_,1'b0};
            3'b101:pp[m1]={A_[8],A_};
            3'b110:pp[m1]={A_[8],A_};
            default:pp[m1]=0;

        endcase
    end
end

assign pp1={{6{pp[0][9]}},pp[0]};
assign pp2={{4{pp[1][9]}},pp[1],2'b0};
assign pp3={{2{pp[2][9]}},pp[2],4'b0};
assign pp4={pp[3],6'b0};
assign pp5={pp[4][7:0],8'b0};
//assign P=pp1+pp2+pp3+pp4;
pp_adder ppa(mask,pp1,pp2,pp3,pp4,pp5,P);//,p1,p2,p3,p4);

endmodule

module pp_adder(input [10:0] mask,
                input [15:0] pp1,
                input [15:0] pp2,
                input [15:0] pp3,
                input [15:0] pp4,
                input [15:0] pp5,
                output [10:0] prod);/
wire [10:0] p1,p2,p3,p4,p5;
assign p1 = pp1[15:5] & mask;
assign p2 = pp2[15:5] & mask;
assign p3 = pp3[15:5] & mask;
assign p4 = pp4[15:5] & mask;
assign p5 = pp5[15:5] & mask;

assign prod=pp1[15:5]+pp2[15:5]+pp3[15:5]+pp4[15:5]+pp5[15:5];
endmodule
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

The verilog implementation of the multiplier without masking is as follows.

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

```

```

module float_mul_maskless(input [0:15] num1,input [0:15] num2,output [0:15] out);

    wire s1,s2;
    wire [0:7] ex1,ex2;
    wire [0:8] m1,m2;

    wire s;
    wire [0:9] exp;
    wire [0:10] mant;
    wire [0:9] exponent;
    wire [0:6] mantissa;

    assign s1=num1[0];
    assign s2=num2[0];
    assign ex1=num1[1:8];
    assign ex2=num2[1:8];
    assign m1={2'b01,num1[9:15]};
    assign m2={2'b01,num2[9:15]};

    sign_exp se(s1,s2,ex1,ex2,s,exp);
    booth_mul bm(m1,m2,mant);
    normal nz(mant,exp,exponent,mantissa);

    assign out={s,exponent[2:9],mantissa};
endmodule

module sign_exp(input s1,input s2,input [0:7] ex1,input [0:7] ex2,output s,output [0:9] exp);
    assign s=s1^s2;
    assign exp={2'b0,ex1}+{2'b0,ex2}-10'd254;
endmodule

module normal(input [0:10] mant,input [0:9] exp,output [0:9] exponent,output [0:6] mantissa);
    assign mantissa=mant[2:8];
    assign exponent=exp+1'b1+10'd127;
endmodule

module booth_mul(input wire [8:0] A,input wire [8:0] B,output wire [10:0] P);

    reg [2:0] bits[4:0];
    reg [9:0] pp[4:0];

    wire [8:0] A_;//minus A
    wire [15:0] pp1;
    wire [15:0] pp2;
    wire [15:0] pp3;
    wire [15:0] pp4;
    wire [15:0] pp5;

```

```

integer m1;
assign A_ = ~A + 1;

always@(A or B or A_) begin

bits[0] = {B[1], B[0], 1'b0};
bits[4] = 3'b001;

for(m1=1; m1<4; m1=m1+1)
    bits[m1] = {B[2*m1+1], B[2*m1], B[2*m1-1]};

for(m1=0; m1<5; m1=m1+1) begin
    case(bits[m1])

        3'b001: pp[m1] = {1'b0, A};
        3'b010: pp[m1] = {1'b0, A};
        3'b011: pp[m1] = {A, 1'b0};
        3'b100: pp[m1] = {A_, 1'b0};
        3'b101: pp[m1] = {A_[8], A_};
        3'b110: pp[m1] = {A_[8], A_};
        default: pp[m1] = 0;

    endcase
end
end

assign pp1 = {6{pp[0][9]}}, pp[0];
assign pp2 = {4{pp[1][9]}}, pp[1], 2'b0;
assign pp3 = {2{pp[2][9]}}, pp[2], 4'b0;
assign pp4 = {pp[3], 6'b0};
assign pp5 = {pp[4][7:0], 8'b0};

assign P = pp1[15:5] + pp2[15:5] + pp3[15:5] + pp4[15:5] + pp5[15:5];

endmodule

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

```


FPGA AND ASIC RESULTS

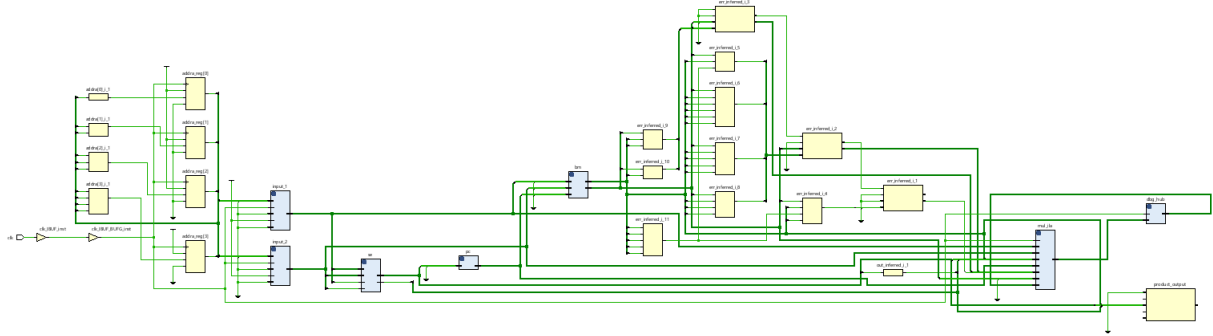


Figure 2: Synthesized result

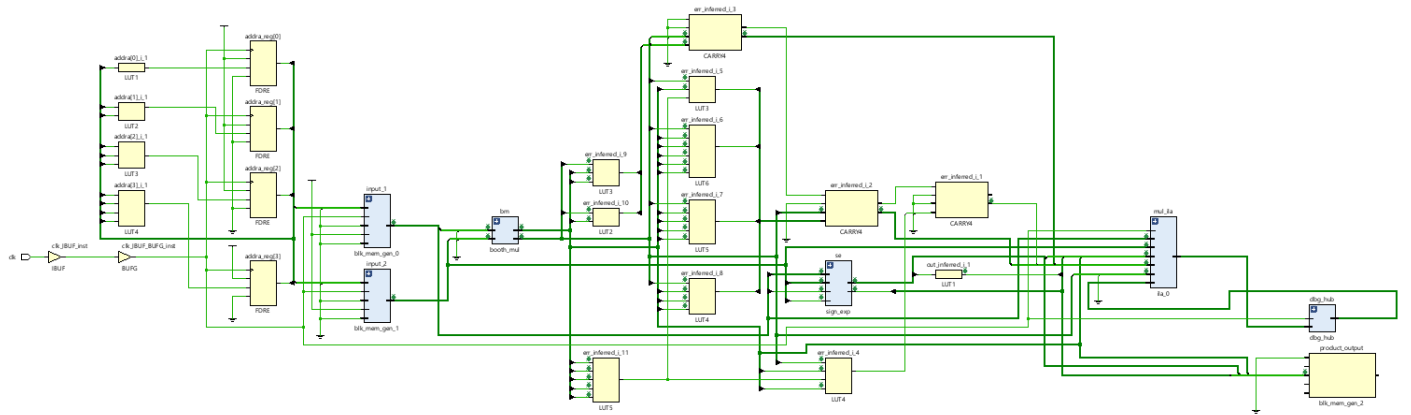


Figure 3: Synthesized Design(without masking)

 


Figure 4: Implemented Result

 


Figure 5: Implementation

Name	^1	Slice LUTs (20800)	Slice Registers (41600)	F7 Muxes (16300)	Slice (8150)	LUT as Logic (20800)	LUT as Memory (9600)	Block RAM Tile (50)	Bonded IOB (106)	BUFGCTRL (32)	BSCANE2 (4)
▼ N top		1609	2376	3	768	1436	173	45	1	2	1
> I bm (booth_mul)		82	0	0	32	82	0	0	0	0	0
> I dbg_hub (dbg_hub)		449	741	0	240	425	24	0	0	1	1
> I input_1 (blk_mem_gen_0)		0	0	0	0	0	0	4.5	0	0	0
> I input_2 (blk_mem_gen_1)		0	0	0	0	0	0	4.5	0	0	0
> I mul_ila (ila_0)		1054	1631	3	520	905	149	36	0	0	0
I pc (prec_ctrl)		5	0	0	3	5	0	0	0	0	0
I product_output (blk_mem_gen_2)		0	0	0	0	0	0	0	0	0	0
I se (sign_exp)		9	0	0	3	9	0	0	0	0	0

Figure 6: Resource Utilisation

Name	^1	Slice LUTs (20800)	Slice Registers (41600)	F7 Muxes (16300)	Slice (8150)	LUT as Logic (20800)	LUT as Memory (9600)	Block RAM Tile (50)	Bonded IOB (106)	BUFGCTRL (32)	BSCANE2 (4)
▼ N top		1484	2286	3	735	1324	160	40	1	2	1
> I bm (booth_mul)		57	0	0	20	57	0	0	0	0	0
> I dbg_hub (dbg_hub)		448	741	0	230	424	24	0	0	1	1
> I input_1 (blk_mem_gen_0)		0	0	0	0	0	0	4.5	0	0	0
> I input_2 (blk_mem_gen_1)		0	0	0	0	0	0	4.5	0	0	0
> I mul_ila (ila_0)		959	1541	3	486	823	136	31	0	0	0
I product_output (blk_mem_gen_2)		0	0	0	0	0	0	0	0	0	0
I se (sign_exp)		9	0	0	3	9	0	0	0	0	0

Figure 7: Resource Utilisation(without masking)

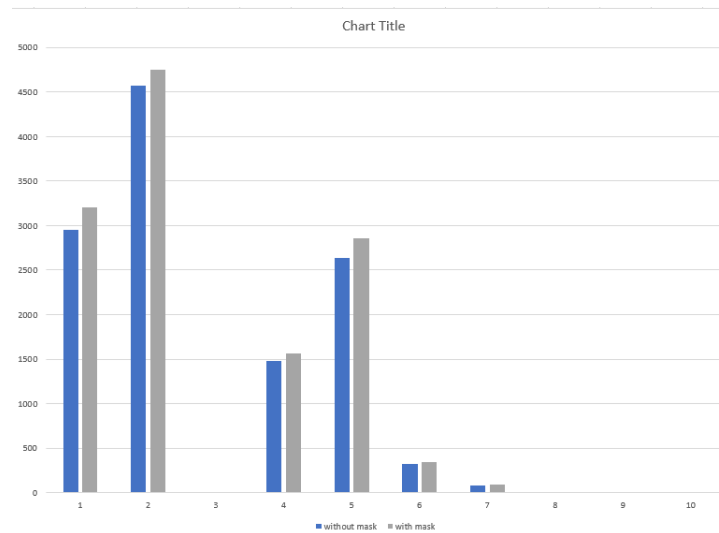


Figure 8: Resource Utilisation Comparison

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.108 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 25.5°C
 Thermal Margin: 59.5°C (11.8 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Medium
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

 


Figure 9: Power

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.112 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 25.6°C
 Thermal Margin: 59.4°C (11.8 W)
 Effective θ_{JA} : 5.0°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Medium
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

 


Figure 10: Power(without masking)

 


Figure 11: Layout

 


Figure 12: Layout(without masking)

```
% box
Root cell box:
      width x height ( llx, lly ), ( urx, ury ) area (units^2)
microns: 125.630 x 136.350 ( 0.000, 0.000), ( 125.630, 136.350) 17129.650
lambda:  12563 x 13635  (   0,  0   ), ( 12563, 13635) 171296505
```

Figure 13: Area

```
% box
Root cell box:
      width x height ( llx, lly ), ( urx, ury ) area (units^2)
microns: 122.840 x 118.890 (-0.390, 7.980), ( 122.450, 126.870) 14604.447
lambda:  12284 x 11889  ( -39, 798 ), ( 12245, 12687) 146044476
```

Figure 14: Area(without masking)

Results

The result utilisation of the multiplier with masking is more than the one without masking. A significant part of it is due to ILA of Vivado. The proposed design however has less power consumption than the one without variable precision approximation. The number of bits to be truncated is decided using the exponent value. The Bit error rate against truncated bit-width is given below.

 


Figure 15: Error vs Truncated bit-width

References

- Variable-Precision Approximate Floating-Point Multiplier for Efficient Deep Learning Computation Hao Zhang , Member, IEEE, and Seok-Bum Ko , Senior Member, IEEE
- J. Han and M. Orshansky, “Approximate computing: An emerging paradigm for energy-efficient design,” in Proc. 18th IEEE Eur. Test Symp. (ETS), May 2013, pp. 1–6.
- Novel, Configurable Approximate Floating-point Multipliers for Error-Resilient Applications Vishesh Mishra¹ , Sparsh Mittal² , Rekha Singhal³ , Manoj Nambiar³ ¹ IIT Kanpur, ² IIT Roorkee, ³TCS Research, India vishesh
- Kaur, Navdeep Patial, Rajeev. (2013). Implementation of Modified Booth Multiplier using Pipeline Technique on FPGA. International Journal of Computer Applications. 68. 38-41. 10.5120/11666-7261.
- Design and Implementation of Radix 4 Based Multiplication on FPGA Supriya S. Sastel¹ Dept. of Electronics Telecommunication Trinity College of Engineering Research Pune,

India. Prof. Anil G. Sawant² Dept. of Electronics Telecommunication Trinity College of Engineering Research Pune, India.

- Implementation of Modified Booth Algorithm (Radix 4) and its Comparison with Booth Algorithm (Radix-2) Sukhmeet Kaur¹, Suman² and Manpreet Singh Manna³ ¹ ECE, SSIET (P.T.U), Derabassi, Punjab, India. ² ECE, SSIET, Derabassi, Punjab, India. ³ EIE, SLIET (Deemed University), Longowal, Sangrur, India.